

DELFT UNIVERSITY OF TECHNOLOGY

MASTER THESIS

MASTER THESIS

Author:

Serwan Asaad

Supervisor:

Dr. Alessandro Bruno

May 18, 2015

Contents

I	Deep-reactive ion etched resonators	3
II	Muxmon experiment	5
1	Muxmon chip architecture	8
2	Qubit characterization	10
2.1	Part I: Continuous-wave measurements	10
2.1.1	Scanning for resonators	11
2.1.2	Powersweeping the resonators	12
2.1.3	Scan for qubit sweet-spots	13
2.1.4	Scanning for qubits	14
2.1.4.1	Spectroscopy	14
2.1.4.2	Avoided crossing	15
2.1.4.3	Tracked spectroscopy	16
2.2	Part II: Time-domain measurements	16
3	Calibration routines	17
4	Randomized benchmarking	18
	Appendices	19
A	Additional notes	20
A.1	Qubit characterization	20
A.1.1	Part I: Continuous-wave measurements	20
A.1.1.1	Powersweep	20
A.1.1.2	Spectroscopy	20
B	Algorithms	21
B.1	Tracked spectroscopy	21
B.2	Peak finding	21
B.3	Compiled RB?	21

INTRODUCTION

Part I

Deep-reactive ion etched resonators

TODO:

- Explain heterodyne detection
- Explain VNA
- Explain that resonance frequency f_r is not necessarily at the transmission minimum when the resonator exhibits asymmetry.

Part II

Muxmon experiment

TODO:

- Explain surface code architecture
- Explain the general structure of a chip:
 - Feedline through which signal is sent and measured
 - CPW resonators, capacitively coupled to feedline
 - Single qubit coupled to resonators (coupling location?)
 - Resonator buses

Introduction

At this moment circuit QED is at the stage where multi-qubit experiments are being realized.

Chapter 1

Muxmon chip architecture

Topics that should be explained in this section:

- The Muxmon0 and Muxmon1 chip are designed with two purposes
 1. Testing multiplexing using the Duplexer
 2. Explore qubit frequency re-use
- Explain similarities of chips
 - Three qubits per chip
 - All three qubits have individual flux tuning
 - Air bridges are used, not only for connect the ground planes, but also such that the feed line can pass over other coplanar waveguides without contact
- Explain differences between Muxmon0 and Muxmon1.
 - The Muxmon0 chip has a driving line connected to each of the qubits. It has two resonator buses at 4.9 GHz and 5.0 GHz. These could also be used for two-qubit gates.

Advantage Able to fully control each qubit individually, even when multiple qubits share the same frequency.

Advantage Less coupling between data qubits.

Disadvantage Requires more driving lines.

Disadvantage Adds extra source of dissipation for the qubits.
 - The Muxmon1 chip has two driving lines, each capacitively coupled to one of the two data qubits, and to the ancilla qubit.

Advantage Less driving lines required

Advantage Less dissipation due to capacitive coupling

Disadvantage Cannot individually control data qubit and ancilla qubit when they share the same frequency

Disadvantage More coupling between qubits

– Simplified model of the surface code

- Explain concepts of cross-coupling and readout cross-talk

Cross-coupling The coupling between qubits.

Cross-coupling leads to transfer of excitation.

An associated coupling strength g can be associated to cross-coupling.

Can be determined by driving one qubit extremely hard, and measuring signal from other qubit.

TODO: Show values of cross-coupling found, or do this in characterization section

TODO: Leads to coherent errors?

TODO: Two types of cross-coupling? Direct leakage of pulse pulse, and transfer of excitation? cross-driving?

Readout cross-talk Coupling between a qubit and a resonator that are not directly coupled.

A part of the signal measured from one resonator is then due to the state of another qubit

TODO: Understand more behind readout cross-talk

Left to think about:

- Should I already include items such as coherence times, the fact that Muxmon0 performs better than Muxmon 1?
- Where should I include coherence times versus frequency?
- Should the part on cross-coupling and readout cross-talk not be in characterization section?
- Should the section on the Duplexer go in here?

Figures that need to be included:

- Muxmon0 and Muxmon1 chip, preferably optical microscopy
 - SEM image of air-bridges such that coplanar wave-guides cross without intersecting
 - schematic of cross-coupling and readout cross-talk
- It could be good to create this using the actual Muxmon chip as background, with arrows indicating how the different effects operate

Chapter 2

Qubit characterization

Description This chapter gives a step-by-step description of how to find a resonator and qubit, and subsequently how to tune the qubit's parameters.

In the design of cQED chips, the parameters of the qubits and resonators are always targeted which are ideal for the experiment. For coplanar waveguide resonators one can already obtain relatively good parameters for the required dimensions from simple formulae **TODO:** refer to formula. For superconducting transmon qubits, however, finding the right dimensions that correspond to the desired parameters is a much more complicated process. The qubit's frequency, for instance, depends on the qubit's coupling energy E_c and Josephson energy E_J . The coupling energy E_c can be reasonably estimated from classical simulations. Finding the right dimensions for the Josephson junction that result in the desired Josephson energy E_J , however, is difficult, and usually physically testing different junctions is necessary to determine an accurate conversion from the desired E_J to the Josephson junction dimensions.

Nevertheless, the actual parameters of the resonators and qubits are almost never where one expects them to be. Once the sample is cooled in the dilution refrigerator, an inevitable game of hide-and-seek follows with the goal of finding the frequency of the resonators and qubits, and subsequently determining their properties. This chapter describes the measurements that were performed to characterize the MuxMon samples.

2.1 PART I: CONTINUOUS-WAVE MEASUREMENTS

Once a sample is properly cooled down it is ready to be measured. At this stage the sample is still an unknown terrain, where the experimenter only has a rough map, containing the sample's targeted parameters, and the specific properties of the resonators and qubits.

The first step is to look for signs of life. These manifest themselves as resonance frequencies of the resonators and the qubits that are coupled to them. As we are not yet interested in the properties of the resonators and qubits which can only be obtained through measurements with accurately timed pulses, we send continuous tones through the feedline, and measure deviations in the transmission. These measurements are known as continuous-wave measurements

2.1.1 Scanning for resonators

Since communication with the qubits is mediated through their coupling to resonators, the first step is to find these resonators. This is done using a transmission measurement, in combination with heterodyne detection, and has been explained in section **TODO**: Create section in Resonator chapter.

There is one difference in measuring a resonator when there is a qubit coupled to it. When considering the qubit as a two-level system, the behaviour of the coupled resonator-qubit system is governed by the Jaynes-Cummings Hamiltonian [1]:

$$\hat{H} = \hbar\omega_r \left(\hat{a}^\dagger \hat{a} + \frac{1}{2} \right) + \frac{\hbar\omega_q}{2} \hat{\sigma}_z + \hbar g \left(\hat{a}^\dagger \sigma_- + \hat{a} \sigma_+ \right) \quad (2.1)$$

where ω_r is the bare resonance frequency of the resonator, ω_q is the resonance frequency of the qubit's ground to excited state transition, and the qubit's two states are in the spin-representation. This Hamiltonian consists of three terms. The first term corresponds to the energy level of the resonator, the second to the energy level of the transmon, and the third is a coupling term between the two with coupling strength g .

The difference between the resonator's frequency ω_r and the qubit's frequency ω_q is given by the detuning $\Delta = \omega_q - \omega_r$. If the magnitude of the detuning is large compared to the coupling strength g , the system is in the dispersive regime. In this case the Hamiltonian can be approximated by the dispersive Jaynes-Cummings Hamiltonian:

$$\hat{H} = \frac{\hbar\omega'_q}{2} \hat{\sigma}_z + \left(\hbar\omega'_r + \hbar\chi \hat{\sigma}_z \right) \hat{a}^\dagger \hat{a} \quad (2.2)$$

The coupling between the qubit and resonator causes both qubit's frequency and the resonator's frequency to shift: $\omega'_q = \omega_q + \chi_{01}$, $\omega'_r = \omega_r - \chi_{12}/2$.

Aside from experiencing a frequency shift dependent on the amount of detuning, Equation 2.2 shows that the resonator also experiences a shift depending on the state of the qubit. The resonator's frequency is decreased by an amount 2χ when the qubit is in the excited state. The parameter χ is the dispersive shift, and is given by:

$$\chi = \chi_{01} - \chi_{12}/2 \approx \frac{g^2}{\Delta} \frac{E_c}{\hbar\Delta - E_c} \quad (2.3)$$

where $\chi_{ij} = \frac{g_{ij}^2}{\omega_{ij} - \omega_c}$ are the partial dispersive shifts.

Due to this coupling between resonator and qubit, it is important to choose the right RF power. When the amount of photons in the resonator reaches a certain point, this coupling will result in the resonator experiencing nonlinear effects. The resonator will thereby lose its Lorentzian lineshape. Therefore the RF power should be kept sufficiently low to avoid these nonlinear effects, while still maintaining a good signal-to-noise ratio.

TODO:

- In the strong coupling regime (Leads to hybridization of qubit and resonator states: quton and fobit)

- Explain that the quality factor is low because the resonator is coupled strongly to the qubit (equation including coupling to qubit?)
- Doesn't χ diverge when $\Delta \rightarrow E_c$?
- explain concept of anharmonicity, and that $\alpha \approx E_c$
- Maybe explain concept of number splitting in dispersive Jaynes-Cummings. Number splitting is the phenomenon that the qubit's frequency shifts by an amount 2χ for every photon in the resonator.
Alternatively mention this in another section.
- Mention that $g_{12} = \sqrt{g}$, and that other coupling strengths are exponentially suppressed in the transmon

Figures:

- Figure of transmission showing all three Muxmon0 resonators

2.1.2 Powersweeping the resonators

Once the resonators have been located, the next stage is to find the qubit that is capacitively coupled to each of the resonators. Instead of directly scanning the entire frequency spectrum in search of the qubit, it is relatively straightforward to perform some initial measurements aimed at gaining information about our resonator and qubit, which will allow us to search for our qubit with much greater accuracy.

As explained previously, the capacitive coupling between the resonator and qubit shifts the resonator frequency ω_r from its bare frequency. When the amount of photons in the resonator reaches a certain point, the resonator experiences nonlinearity, thereby losing its Lorentzian lineshape. When increasing the RF power even further, at a certain point the resonator regains its Lorentzian lineshape. In doing so its resonance frequency has shifted to its bare frequency ω_{bare} . If this frequency shift is observed, it indicates that the resonator's frequency was shifted, and hence that the qubit is alive. Measuring this frequency shift is commonly done in a powersweep. A powersweep is a measurement in which a resonator scan is performed for a range of powers.

A powersweep additionally provides information about at what power the resonator enters the nonlinear regime. For measurements involving the qubit the readout power must be below this threshold power. Furthermore, from the frequency shift between the dressed cavity frequency and the bare cavity frequency, the amount of detuning between the qubit and the resonator can be estimated using Equation 2.3.

If no shift is observed, it could mean that the qubit is dead (e.g. because the Josephson junction is shorted). However, this is not necessarily the case. An alternative possibility is that the detuning between qubit and resonator is very large, and as a result the frequency shift cannot be discerned. At this point it is too early to draw conclusions, and we may almost draw the analogy with Schrödinger's cat in a box.

TODO:

- Explain theory behind transition to bare cavity frequency (Reed's thesis has some information)

Figures:

- Powersweep of ancilla qubit

2.1.3 Scan for qubit sweet-spots

Some of the qubits have a tunable resonance frequency. This is done through a superconducting quantum interference device (SQUID). In this case the two islands that compose the transmon qubit are connected by two Josephson junctions instead of one, effectively forming a loop. The SQUID loop is sensitive to the amount of flux passing through the loop. The amount of flux going through the SQUID loop can be changed by changing the surrounding magnetic field. This is commonly done by having a flux bias line in close proximity to the SQUID loop. Current flowing through the flux-bias line alters the magnetic field in the vicinity of the SQUID loop, and hence changes the amount of flux through the SQUID loop. A digital-to-analog converter is used to specify the amount of current that is sent through the flux bias line. Depending on the amount of flux through the SQUID loop, the resonance frequency of the qubit changes accordingly. These qubits are therefore called flux-tunable.

For qubits that are flux-tunable, finding the sweet-spot of the qubit can be done without knowledge of the qubit's frequency. This can be done by sweeping the DAC voltage and measuring the shift in the resonance frequency. Because the frequency of the qubit varies as the amount of current through the flux-bias line changes, the detuning between the qubit and the resonator consequently changes. As a result the dispersive shift χ , and therefore the resonator's frequency, also varies. At the sweet-spot of the qubit, the resonator's frequency ω_r is at a maximum. This is irrespective of whether the qubit's frequency ω_q is above or below the resonator's frequency.

The accurate way to measure the sweet-spot is to perform resonator scans as the DAC voltage is varied. The result is a 2D scan shown in **TODO: Figure**.

A faster second approach for finding the qubit sweet-spot, at the cost of providing less information, is by choosing a fixed frequency close to the resonator's frequency ω_r (preferably slightly below, where the transmission slope is steepest). By measuring the amount of transmission as the DAC voltage is being varied, one obtains essentially a line-cut of **TODO: Figure**. The idea this measurement is that if the qubit's frequency f_q decreases, the resonator's frequency also decreases, resulting in a decrease in transmission (closer to ω_r). Likewise, if the qubit's frequency ω_q increases, the resonator's frequency increases **TODO: Why?**, resulting in an increase in transmission (further away from ω_r).

At the qubit's sweet-spot, the resonator's frequency ω_r is at a maximum, and so the transmission should also be at a maximum. Furthermore, because the amount of detuning only depends on the deviation from the flux sweet-spot **TODO: improve**, the transmission should be symmetric with respect to the DAC voltage sweet-spot. If the resonator's frequency ω_r shifts by a large amount in the course of this measurement, it becomes harder to determine where the sweet-spot is (although even then often it can still be discerned). Nevertheless,

this method is considerably faster than performing a full two-dimensional scan of frequency versus DAC voltage, and in most cases it works like a charm.

In the case where the powersweep showed no measurable frequency shift, these two measurements are also useful in discerning whether or not the qubit is actually dead, or whether it was simply far detuned from the resonator.

TODO:

- Explain how qubit's frequency has a cosine dependence on DAC
- Give detailed information on SQUID loop
 - Why does the qubit frequency change in a SQUID loop
 - Sweet-spot
- Mention flux-noise?
 - 1/f noise
 - usually not limiting, as it is very slow
 - This noise can be seen as occasional jumps (every few hours?) It would mean that every few hours the frequency must be recalibrated.

Figures:

- SEM picture of SQUID loop, including flux-bias line
- Figure of 2D resonator scan vs DAC voltage
- Figure of 1D resonator fixed frequency DAC voltage scan

2.1.4 Scanning for qubits

Once the preliminary measurements have been performed that characterize the resonators and provide hints about the whereabouts of the qubit it is time to actually find the qubit.

The measurement to perform in order to find the qubit depends on the amount of detuning between the resonator and qubit, which can be estimated from powersweep measurements. If the amount of detuning is large compared to the coupling strength ($\Delta \gg g$), the system is in the dispersive regime. In this case one commonly performs a two-tone spectroscopy to find the qubit's frequency.

2.1.4.1 Spectroscopy

As was explained in section 2.1.1 the resonator experiences a 2χ frequency shift dependent on the state of the qubit. In the case of a resonator capacitively coupled to the feedline, the transmission experiences a dip at the resonator's frequency. This dip will correspondingly shift when the qubit's state is swapped. The transmission at the resonator's dip when the qubit is in the ground state will be dependent on the state of the qubit (low when the qubit is

in the ground state, high when the qubit is in the excited state). This is the property exploited in a two-tone spectroscopy measurement.

In a two-tone spectroscopy measurement two tones are sent through the feedline.

1. A measurement tone at the resonator's frequency when the qubit is in the ground state.
2. A drive tone with varying frequency ω_d .

The transmission through the feedline is measured while the frequency of the drive tone ω_d is swept. When the drive frequency ω_d is detuned from the qubit's frequency ω_q , the drive is off-resonant with respect to the qubit, and so we measure a low transmission. However, when the drive frequency ω_d approaches the qubit's frequency ω_q , then the qubit will start to oscillate between its ground and excited state, with a rate dependent on the detuning between the drive frequency ω_d and the qubit's frequency ω_q . The minimum linewidth of the qubit using spectroscopy is set by its dephasing time T^2 , which can be seen as the uncertainty in its frequency. However, the power of the drive tone causes an additional increase in the linewidth, due to stimulated emission of the qubit. This effect is known as power broadening. This effect can be quite useful for finding qubits, especially when designing high-quality qubits with a very narrow intrinsic linewidth.

TODO: Spectroscopy section

- Detuning
- Spectroscopy tone or drive tone?
- Drive strength (see Reed's thesis p115)
- Is power broadening really due to stimulated emission?
- Explain optimal RF power
- tracked spectroscopy?

2.1.4.2 Avoided crossing

When the qubit's frequency is close to that of the resonator, the two experience a strong coupling **TODO:** Why?

Avoided crossing info:

- Actually the threshold is determined by the ratio between detuning and coupling strength
- The coupling strength g is the minimum distance between the splitting

- From Reed's thesis p.63 explanation of this avoided crossing is given

$$E_0 = -\frac{\hbar\Delta}{2} \quad (2.4)$$

$$E_1 = n\hbar\omega_r \pm \frac{\hbar}{2}\sqrt{4g^2n + \Delta^2} \quad (2.5)$$

Joining $E_0 + E_1$ results in a qubit approaching a resonator from the top. When the frequency of the qubit equals that of the resonator, the energy difference reaches a minimum, and is equal to $2g$.

TODO:

- Explain the quton fobit behaviour near the avoided crossing
- Explain how one can extract coupling from avoided crossing

figures:

- Figure of avoided crossing

If the qubit is flux-tunable, one important question to ask is: at what DAC voltage should the qubit be searched?

There are several options. The first option is to choose zero DAC voltage. In most cases this is alright, but there are cases when this is a bad choice. For instance, due to trapped magnetic fields during cool-down the qubit could be positioned at the anti-sweet-spot for zero DAC voltage, in which case finding the qubit will be next to impossible.

A better option is to choose a DAC voltage depending on the amount of detuning previously measured. Ideally either a few hundred megahertz or zero.

TODO:

- Use relatively high source power, results in power broadening
- Mention what to do if qubit is close to or far away from resonator
- Mention the term transmission measurement earlier on.
- Pulsed spectroscopy

2.1.4.3 Tracked spectroscopy

2.2 PART II: TIME-DOMAIN MEASUREMENTS

Chapter 3

Calibration routines

Chapter 4

Randomized benchmarking

Appendices

Appendix A

Additional notes

A.1 QUBIT CHARACTERIZATION

A.1.1 Part I: Continuous-wave measurements

A.1.1.1 Powersweep

- If the resonator seems to disappear after the transition from dressed frequency to bare frequency (or vice versa), this is likely due to the qubit being extremely close to the resonator, and so the frequency shift is large.

A.1.1.2 Spectroscopy

- If the deviation in transmission becomes less due to more detuning, increasing the power can also increase the contrast.

Appendix B

Algorithms

B.1 TRACKED SPECTROSCOPY

B.2 PEAK FINDING

B.3 COMPILED RB?

Bibliography

- [1] Matthew D. Reed. *Entanglement and Quantum Error Correction with Superconducting Qubits*, year =. PhD thesis.